

# CSE216 Programming Abstractions

## Event Driven Simulation

YoungMin Kwon

# Event-driven Simulation


- Event-driven simulation
  - An **action (event) triggers further events** that happens at a later time
  - Those events trigger more events, and so on

# Event-driven Simulation

- Typical architecture
  - Event **generators** have a **list of event callback** procedures
  - Event **receiver registers** its event **callback** to the generator's list
  - When a generator **fires an event**, all event **callback** procedures are invoked
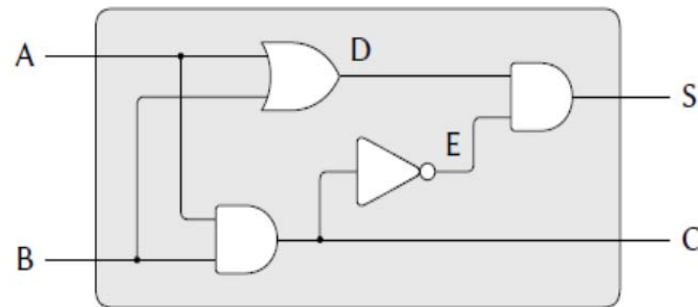
# Digital Circuit Simulator

- Wires
  - Carry digital signals (0 and 1)
  - Function as **event generator**
  - When its signal **value is changed**, its registered **callback** procedures (gates) are invoked




A half-adder circuit.

# Digital Circuit Simulator

- Logical gates


- Inverter, and-gate, or-gate

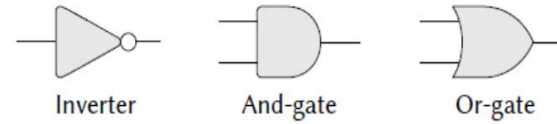

- Connect wires

- Produce output signals computed from input signals

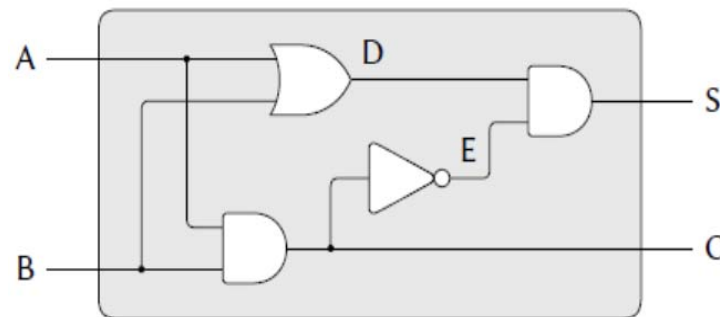
- Output signal is **delayed** by a time dependent on the gate



A half-adder circuit.
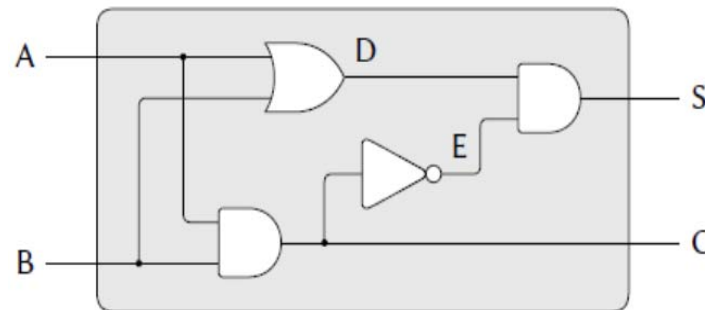
# Digital Circuit Simulator


- Logical gates
  - Functions as **event receiver**
  - Registers its **callback** procedure to **input wire(s)**
  - When the **callback is invoked**, it updates the signal value of the **output wire**



A half-adder circuit.
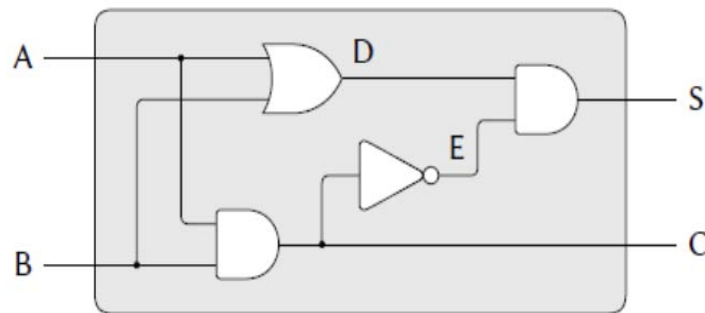
# Digital Circuit Simulator

- Half adder
  - Adds two bits A and B
  - Produces their sum and carry




A half-adder circuit.

Inputs		Outputs	
A	B	C	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0
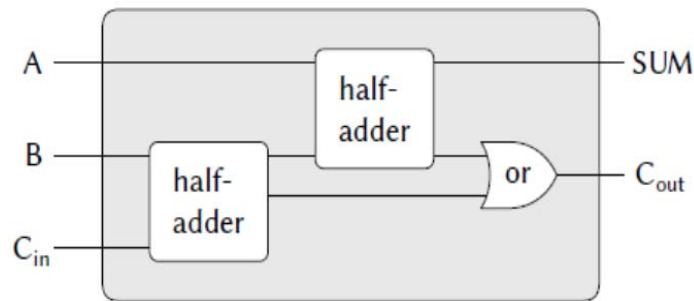
# Digital Circuit Simulator

- Full adder
  - Adds three bits  $A$ ,  $B$ , and  $C_{in}$
  - Produces their sum and carry ( $C_{out}$ )



A full-adder circuit.

Inputs			Outputs	
A	B	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# Digital Circuit Simulator

- n-bit Ripple-carry adder
  - Adds n-bit binary numbers

